


Chapter 5 :: Digital Building Blocks

Digital Design and Computer Architecture

David Money Harris and Sarah L. Harris

Chapter 5 :: Topics

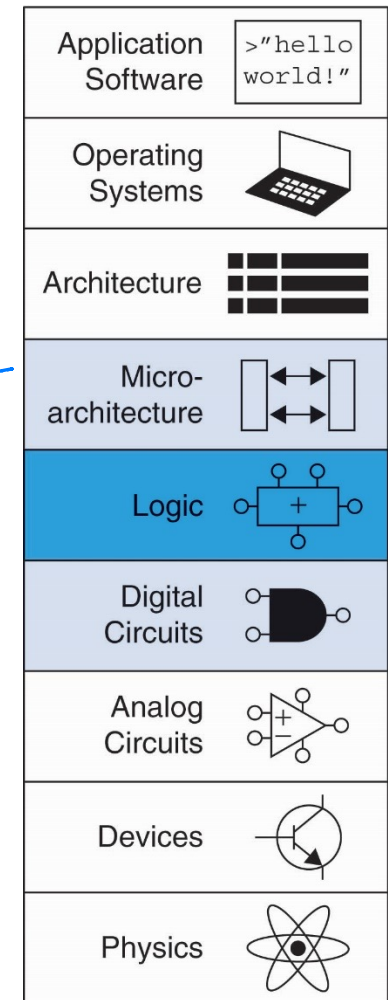- 5.1 Introduction
- 5.2 Arithmetic Circuits
- 5.3 Number Systems
- 5.4 Sequential Building Blocks
- 5.5 Memory Arrays
- 5.6 Logic Arrays




5.1 Introduction

- Digital building blocks:
 - Gates, multiplexers, decoders, registers, arithmetic circuits, counters, memory arrays, logic arrays
- Building blocks demonstrate hierarchy, modularity, and regularity:
 - Hierarchy of simpler components
 - Well-defined interfaces and functions
 - Regular structure easily extended to different sizes
- Will use many of these building blocks to build a microprocessor in Chapter 7

5.2 Arithmetic Circuit

1-Bit Adders


Half Adder

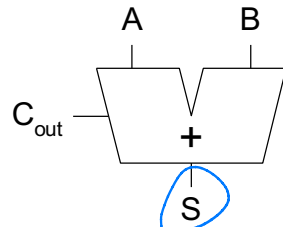

A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

S =
C_{out} =

Full Adder

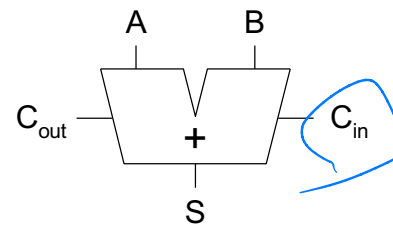

C _{in}	A	B	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

S =
C_{out} =

Handwritten addition for Half Adder:


$$\begin{array}{r} A \\ + B \\ \hline C_{out} \quad S \end{array}$$

Handwritten addition for Full Adder:

$$\begin{array}{r} C_{in} \quad 0 \\ A \quad 1 \\ + B \quad 1 \\ \hline C_{out} \quad S \end{array}$$

1-Bit Adders

Half Adder

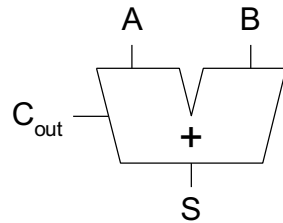


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$



Full Adder

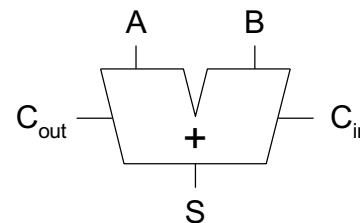


C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + BC_{in} + AC_{in}$$

1-Bit Adders

Half Adder

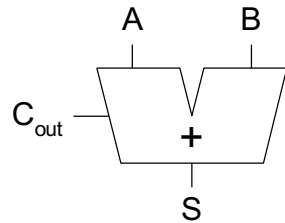


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

Full Adder

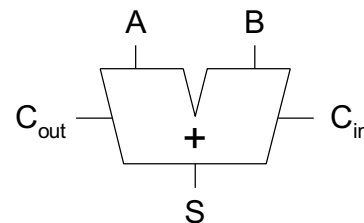

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

Multibit Adder, also called CPA

- Several types of carry propagate adders (CPAs) are:
 - Ripple-carry adders (slow)
 - Carry-lookahead adders (fast)
 - Prefix adders (faster)
- Carry-lookahead and prefix adders are faster for large adders but require more hardware.

Symbol

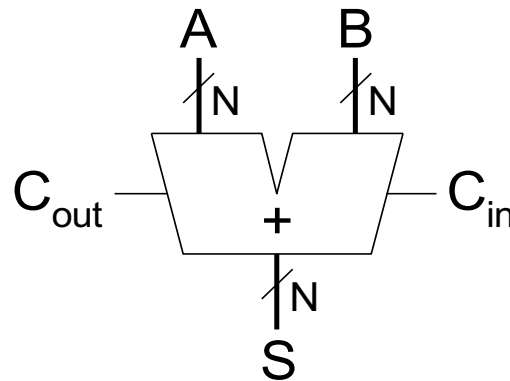


*N = any
integer
number*

Ripple-Carry Adder

- Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**

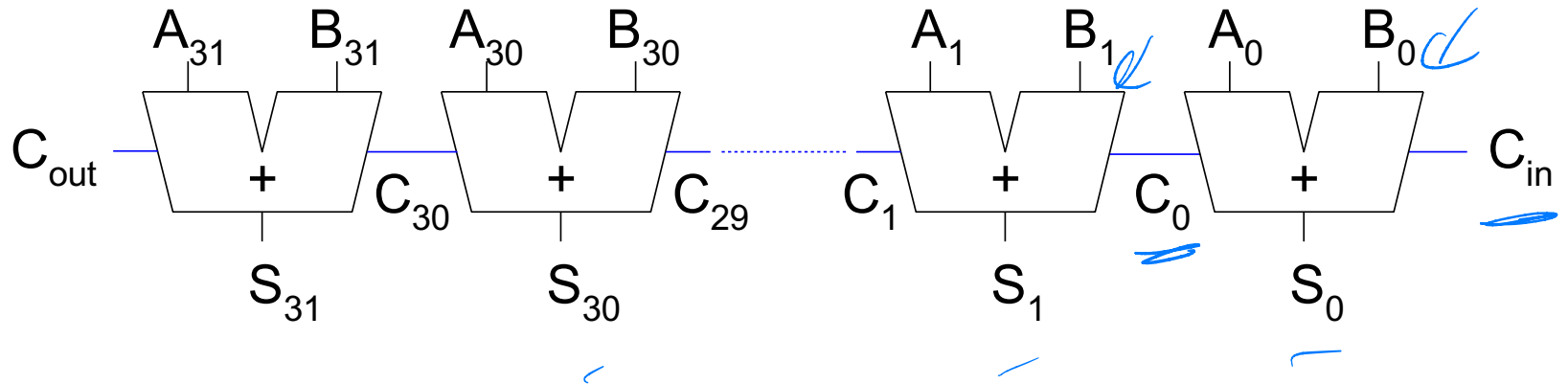
$$\begin{array}{r}
 C_2 \ C_1 \ C_0 \ C_{in} \\
 A_3 \ A_2 \ A_1 \ A_0 \\
 + \ B_3 \ B_2 \ B_1 \ B_0 \\
 \hline
 C_{out} \ S_3 \ S_2 \ S_1 \ S_0
 \end{array}$$




5.2.2 Subtractor

$$A - B = A + (-B)$$

Symbol

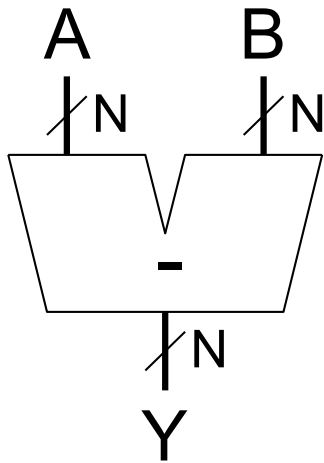


Implementation

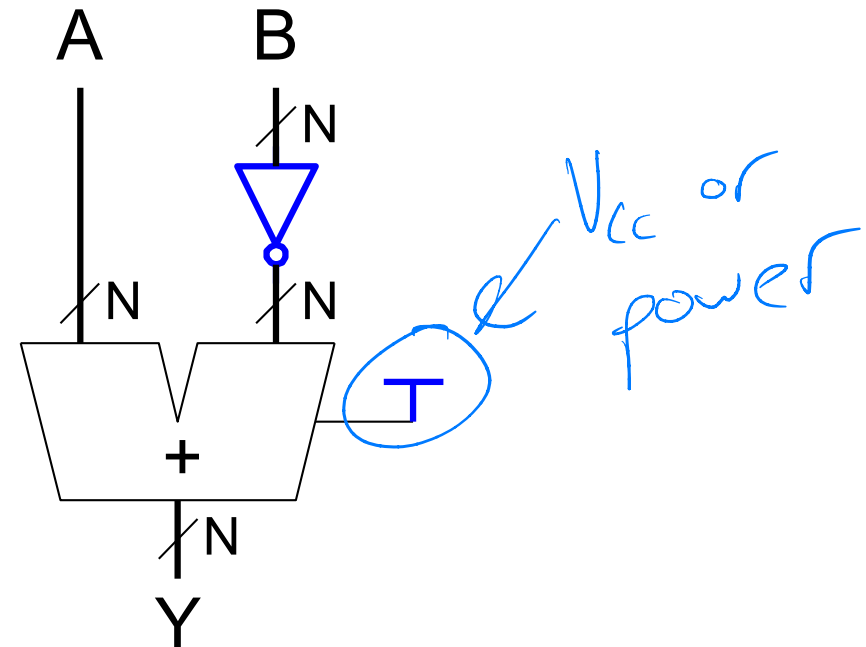


5.2.3 Comparator: Equality

Symbol

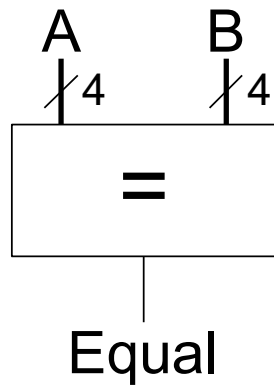


Implementation

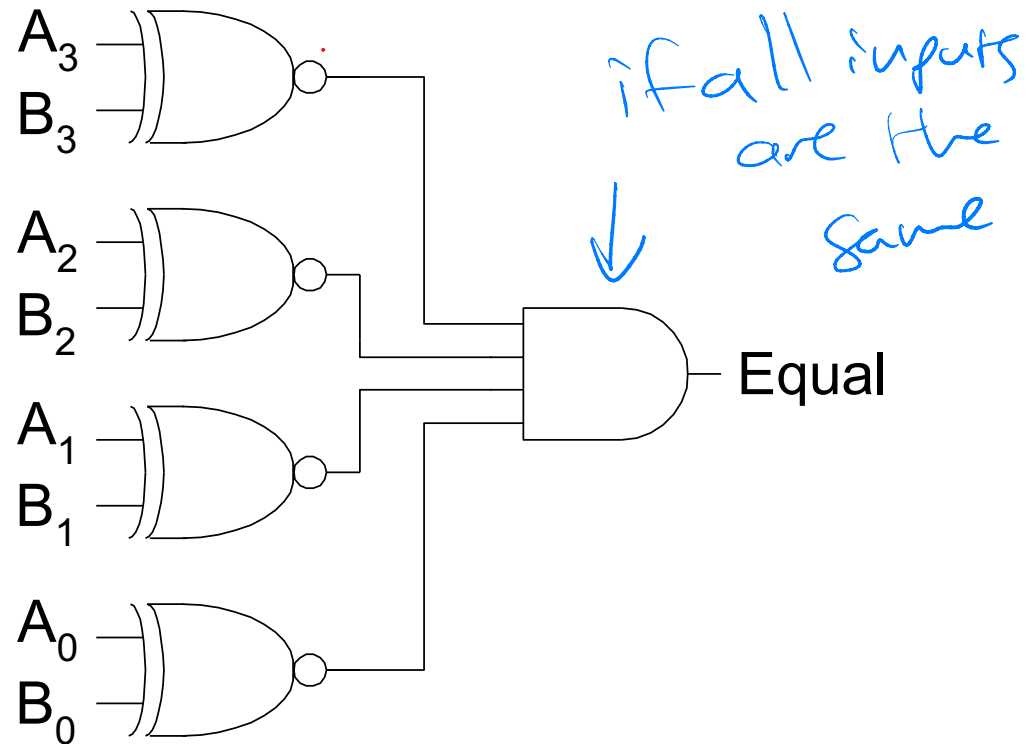

5.2.4 Arithmetic Logic Unit (ALU)

→ 111111 0000000000

define the operation
↓

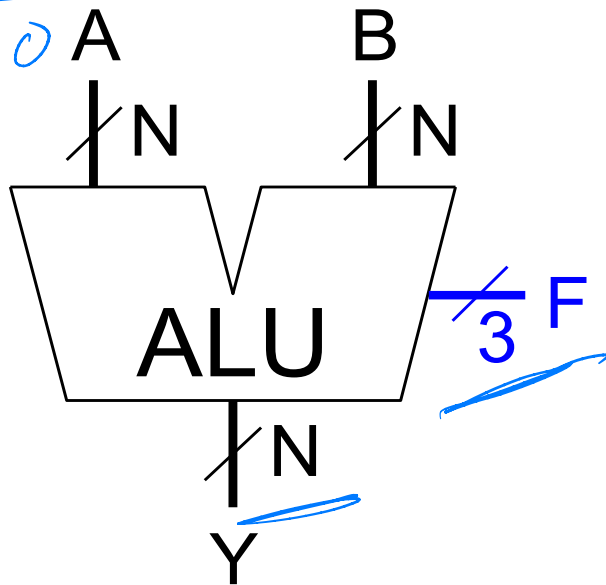

bitwise operations

F _{2:0}	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & <u>~</u> B
101	A <u>~</u> B
110	A - B
111	SLT

AND

OR

ADD

SUB

Defined in Lab 2

true : if A < B
false otherwise

← set if less than

5.2.5 Shifters

- **Logical shifter:** shifts value to left or right and fills empty spaces with 0's

– Ex: $11001 \gg 2 = 00110$

– Ex: $11001 \ll 2 = 00100$

bits represent a numeric value

- **Arithmetic shifter:** same as logical shifter, but on right shift, fills empty spaces with the old most significant bit (msb).

– Ex: $11001 \ggg 2 = 11100$

– Ex: $11001 \lll 2 = 00100$

- **Rotator:** rotates bits in a circle, such that bits shifted off one end are shifted into the other end

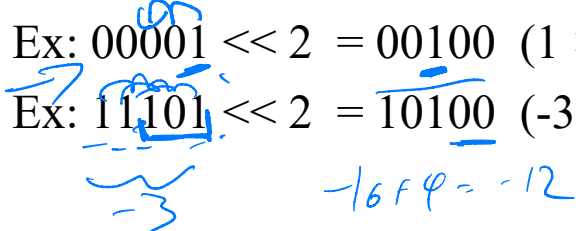

– Ex: $11001 \text{ ROR } 2 = 01100$

– Ex: $11001 \text{ ROL } 2 = 00111$

Shifters

- **Logical shifter:** shifts value to left or right and fills empty spaces with 0's
 - Ex: $11001 \gg 2 = 00110$
 - Ex: $11001 \ll 2 = 00100$
- **Arithmetic shifter:** same as logical shifter, but on right shift, fills empty spaces with the old most significant bit (msb).
 - Ex: $11001 \ggg 2 = 11110$
 - Ex: $11001 \lll 2 = 00100$
- **Rotator:** rotates bits in a circle, such that bits shifted off one end are shifted into the other end
 - Ex: $11001 \text{ ROR } 2 = 01110$
 - Ex: $11001 \text{ ROL } 2 = 00111$

Shifters as Multipliers and Dividers

- A left shift by N bits multiplies a number by 2^N
 - Ex: $00001 \ll 2 = 00100$ ($1 \times 2^2 = 4$)
 - Ex: $11101 \ll 2 = 10100$ ($-3 \times 2^2 = -12$)

- The arithmetic right shift by N divides a number by 2^N
 - Ex: $01000 \ggg 2 = 00010$ ($8 \div 2^2 = 2$)
 - Ex: $10000 \ggg 2 = 11100$ ($-16 \div 2^2 = -4$)


5.3 Number Systems

- What kind of numbers do you know ?
- How to represent using binary representations?
 - Positive numbers
 - Unsigned binary
 - Negative numbers
 - Two's complement
 - Sign/magnitude numbers
- What about fractions?

fixed point

$$\begin{array}{cccc} \frac{1}{2} & \frac{1}{4} & \frac{1}{8} & \frac{1}{16} \\ \uparrow & \uparrow & \uparrow & \uparrow \\ \frac{1}{2^1} & \frac{1}{2^2} & \frac{1}{2^3} & \frac{1}{2^4} \end{array}$$


5-<15>

5.4 Sequential Building Blocks

5.4.1 Counters


- Increments on each clock edge.
- Used to cycle through numbers. For example,
 - 000, 001, 010, 011, 100, 101, 110, 111, 000, 001...
- Example uses:
 - Digital clock displays
 - Program counter: keeps track of current instruction executing

Symbol

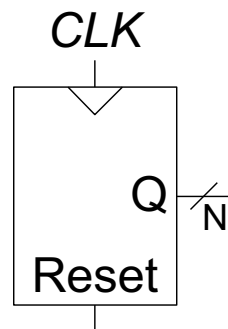

register →

Implementation

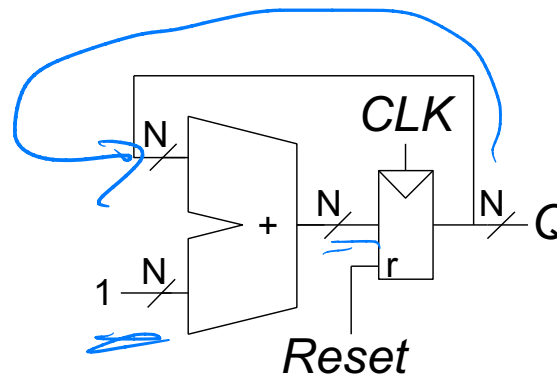

0001